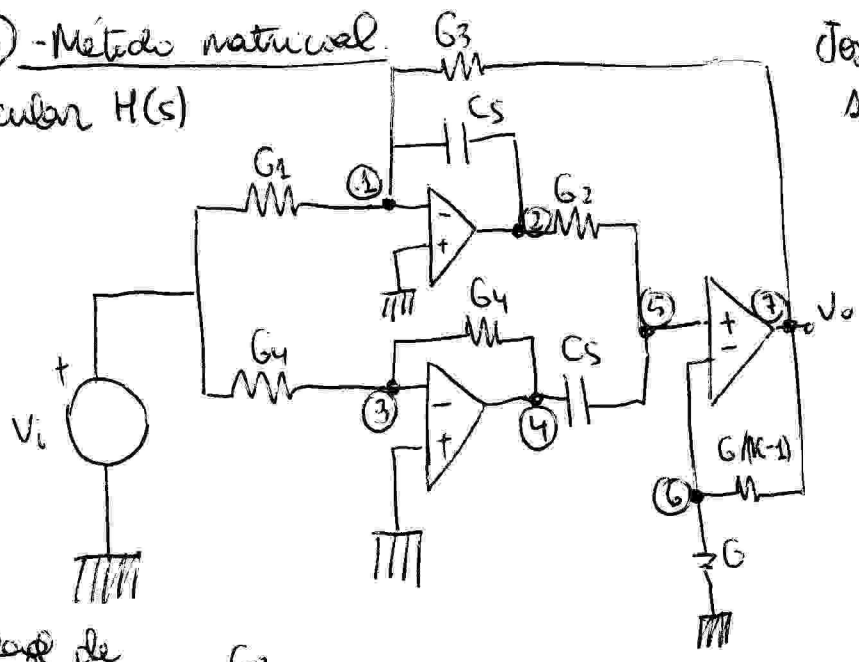


② - Método matricial.



\*) Calcular  $H(s)$

José Antonio Sáez Muñoz  
1º Ingeniería Informática  
FTC



Realimentación negativa.

Modulos de generadores:

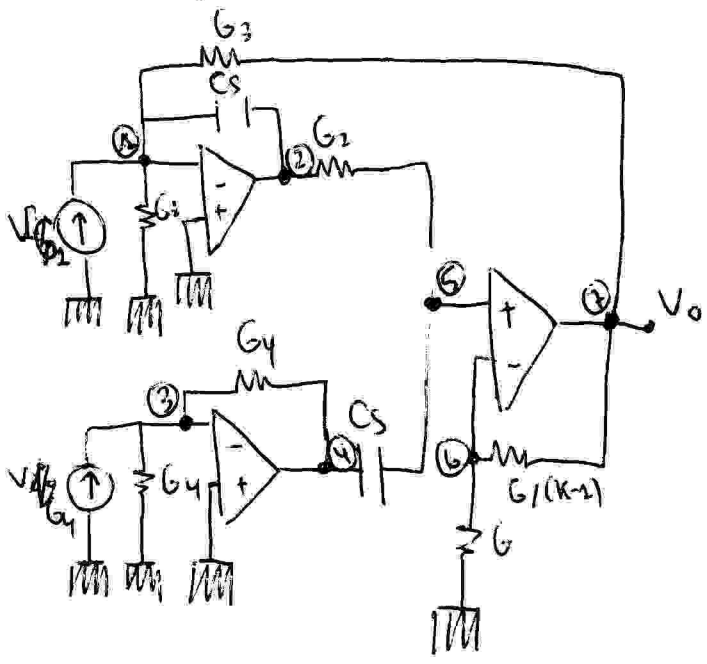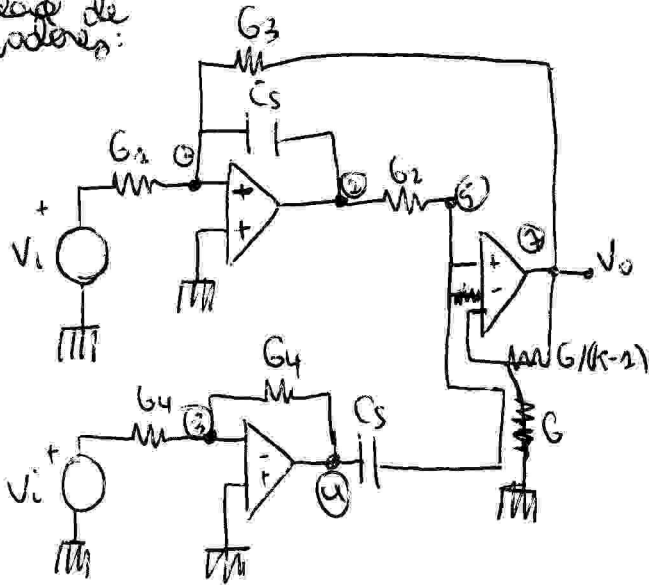

$$\begin{array}{ccccccc|cccc}
 G_2 + C_5 + G_3 & -C_5 & 0 & 0 & 0 & 0 & -G_3 & \cancel{V_1} & \cancel{V_2} & \cancel{V_1 G_2} \\
 -C_5 & G_2 + G_3 & 0 & 0 & -G_2 & 0 & 0 & \cancel{V_3} & \cancel{V_4} & V_1 G_4 \\
 0 & 0 & 2G_4 & -G_4 & 0 & 0 & 0 & V_4 & = & \cancel{V_5} \\
 0 & 0 & -G_4 & G_4 + C_5 & -C_5 & 0 & 0 & V_5 & & 0 \\
 0 & -G_2 & 0 & -C_5 & G_2 + C_5 & 0 & 0 & \cancel{V_6} & & 0 \\
 0 & 0 & 0 & 0 & \cancel{G_2 + C_5} & \cancel{G_2 + C_5} & \frac{G}{K-1} + G & \frac{-G}{K-1} & & 0 \\
 -G_3 & 0 & 0 & 0 & 0 & 0 & -G & \frac{G_3 + G}{K-1} & & \cancel{V_7}
 \end{array}$$

$$V_1 = 0$$

$$V_3 = 0$$

Nodo salida  $\rightarrow V_2$

Nodo salida  $\rightarrow V_4$

Nodo salida  $\rightarrow V_7$

$$V_5 = V_6$$

$$A = \begin{pmatrix} -C_5 & 0 & 0 & -G_3 \\ 0 & -G_4 & 0 & 0 \\ -G_2 & -C_5 & G_2 + C_5 & 0 \\ 0 & 0 & \frac{G}{K-1} + G & \frac{-G}{K-1} \end{pmatrix} \begin{pmatrix} V_2 \\ V_4 \\ V_5 \\ V_7 \end{pmatrix} = \begin{pmatrix} V_1 G_2 \\ V_1 G_4 \\ 0 \\ 0 \end{pmatrix}$$

$$V_7 = \frac{\begin{vmatrix} -C_5 & 0 & 0 & V_i G_1 \\ 0 & -G_4 & 0 & V_i G_4 \\ -G_2 & -C_5 & G_2 + C_5 & 0 \\ 0 & 0 & \frac{G}{K-1} + G & 0 \end{vmatrix}}{\det(A)} = \det(B)$$

$$|A| = \begin{vmatrix} -C_5 & 0 & 0 & -G_3 \\ 0 & -G_4 & 0 & 0 \\ -G_2 & -C_5 & G_2 + C_5 & 0 \\ 0 & 0 & \frac{G}{K-1} + G & \frac{-G}{K-1} \end{vmatrix}$$

$$|A| = (-G_4) \cdot A_{22} = -G_4 \cdot (-1)^{2+2} \begin{vmatrix} -C_5 & 0 & -G_3 \\ -G_2 & G_2 + C_5 & 0 \\ 0 & \frac{G}{K-1} + G & \frac{-G}{K-1} \end{vmatrix} = -G_4 \left( (-C_5 G_2 - C_5^2) \left( \frac{-G}{K-1} \right) + G_2 G_3 \left( \frac{G}{K-1} + G \right) \right)$$

$$|A| = -G_4 \left( \frac{C_5 G_2 G}{K-1} + \frac{C_5^2 G}{K-1} + \frac{G_2 G_3 G}{K-1} + G G_2 G_3 \right)$$

$$|B| = \left( \frac{G}{K-1} + G \right) A_{43} = \left( \frac{G}{K-1} + G \right) (-1)^{4+3} \begin{vmatrix} -C_5 & 0 & V_i G_2 \\ 0 & -G_4 & V_i G_4 \\ -G_2 & -C_5 & 0 \end{vmatrix} = \left( \frac{G}{K-1} + G \right) \left( -G_2 G_4 V_i G_2 + C_5^2 V_i G_4 \right)$$

$$V_3 = V_7 = \frac{\left( \frac{G}{K-1} + G \right) (G_2 G_4 V_i G_2 + C_5^2 V_i G_4)}{G_4 \left( \frac{C_5 G_2 G}{K-1} + \frac{C_5^2 G}{K-1} + \frac{G_2 G_3 G}{K-1} + G G_2 G_3 \right)}$$

$$V_o = \frac{\left(\frac{G}{K-1} + \frac{G(K-1)}{K-1}\right) (G_2 G_4 V_i G_1 + C^2 s^2 V_i G_4)}{G_4 \left( \frac{C s G_2 G + C^2 s^2 G + G_2 G_3 G + G G_2 G_3 (K-1)}{K-1} \right)}$$

$$V_o = \frac{\left(\frac{G + G(K-1)}{K-1}\right) (G_2 G_4 V_i G_1 + C^2 s^2 V_i G_4) (K-1)}{G_4 C s G_2 G + G_4 C^2 s^2 G + G_2 G_3 G_4 + G G_2 G_3 G_4 (K-1)}$$

$$V_o = \frac{\cancel{G} \cdot (\cancel{K} + \cancel{K} - \cancel{K}) (G_2 V_i G_1 + C^2 s^2 V_i)}{C s G_2 \cancel{G} + C^2 s^2 \cancel{G} + G_2 G_3 \cancel{G} + \cancel{G} G_2 G_3 (K-1)} = \frac{G_2 V_i G_1 K + C^2 s^2 V_i K}{C s G_2 + C^2 s^2 + G_2 G_3 + G_2 G_3 K - G_2 G_3}$$

$$V_o = \frac{G_2 V_i G_1 K + C^2 s^2 V_i K}{C s G_2 + C^2 s^2 + G_2 G_3 K} = V_i \left( \frac{G_2 G_1 K + C^2 s^2 K}{C s G_2 + C^2 s^2 + G_2 G_3 K} \right)$$

$$\frac{V_o}{V_i} = \frac{G_2 G_1 K + C^2 s^2 K}{C s G_2 + C^2 s^2 + G_2 G_3 K}$$

Seguros que está bien !