



ANÁLISIS DE CIRCUITOS

1º Ingeniería en Telecomunicación Soluciones de la 5ª Relación de problemas

1. a) $V_T = V_s RC_1 s / (1 + RC_1 s)$, $Z_T = 1/C_2 s + R / (1 + RC_1 s)$
b) $V_T = V_s (R^2 C^2 s^2 + 2RCs + 1) / (R^2 C^2 s^2 + 3RCs + 1)$, $Z_T = R(2RCs + 1) / (R^2 C^2 s^2 + 3RCs + 1)$
2. $f_c = 0.35/t_r$
3. Oscilante amortiguada, con $f = 1.584 \text{ MHz}$ y $\tau = 1 \mu\text{s}$
4. $v_0(t) = t/RC - 0.5(1 - \exp(-t/0.6RC))$
- 5.
- 6.
7. $\omega_{\max} = 10^3 \text{ s}^{-1}$, $T_{\max} = -9.54 \text{ dB}$
- 8.
- 9.
10. $(y) = (z)^{-1}$
11. z: $h_{11}, 0, -h_{21}/h_{22}, 1/h_{22}$; y: $1/h_{11}, 0, h_{21}/h_{11}, h_{22}$; g: $1/h_{11}, 0, -h_{21}/h_{11}h_{22}, 1/h_{22}$
12. $Y = 1/3Z$
13. a) $v_s z_{21} / (R_s + z_{11})$, $(\Delta_z + R_s z_{22}) / (z_{11} + R_s)$; b) $-y_{21} v_s / (y_{22} + R_s \Delta_y)$, $(1 + R_s y_{11}) / (y_{22} + R_s \Delta_y)$; c) $-h_{21} v_s / \Delta_h$, h_{11} / Δ_h